

Figure 1: Enter Caption




Name: B SHAMALA DEVI

Batch: COMETFWC030

Date: 30-june-2025

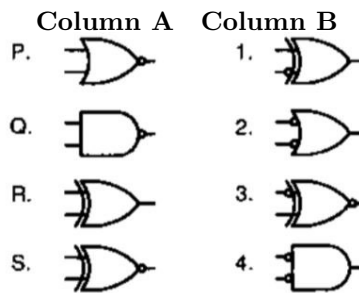**Q.11 Match the logic gates in Column A with their equivalents in Column B**



(A) P-2, Q-4, R-1, S-3

(C) P-2, Q-4, R-3, S-1

(B) P-4, Q-2, R-1, S-3

(D) P-4, Q-2, R-3, S-1

**Q11. Match the logic gates in Column A with Column B**

**Column A:**

- P – OR gate: outputs 1 if any input is 1.
- Q – AND gate: outputs 1 only if both inputs are 1.
- R – NOR gate: outputs 1 only if both inputs are 0 (NOT of OR).
- S – XOR gate: outputs 1 if inputs are different.

**Column B:**

1. NOR gate – OR gate followed by a NOT.
2. AND gate – basic multiplication logic.
3. XOR gate – exclusive OR: outputs 1 if inputs differ.
4. OR gate – outputs 1 if any input is 1.

**Explanation:**

[leftmargin=2em]P is an OR gate  $\rightarrow$  matches with 4. Q is an AND gate  $\rightarrow$  matches with 2. R is a NOR gate  $\rightarrow$  matches with 1. S is an XOR gate  $\rightarrow$  matches with 3.

**Correct Matching:** P-4, Q-2, R-1, S-3 **Answer: (B)**